

Concept Question 4-1: In the s -domain, initial conditions associated with capacitors and inductors are represented by equivalent voltage sources or current sources. Are such voltage sources connected in series with the circuit element or in parallel with it? What about equivalent current sources, how are they connected?

Voltage sources are connected in series with the circuit element, whereas the current sources are connected in parallel with the circuit element. See Table 4-1.